 


Frequency Dividers

Professor Jri Lee

台大電子所 李致毅教授




Electrical Engineering Department
National Taiwan University

Outline


- ❑ **Introduction**
- ❑ **Static Dividers**
- ❑ **Miller Dividers**
- ❑ **Injection Dividers**
- ❑ **Prescalers**
- ❑ **Case Study**

Full-Rate Divider Applications

Broadband Receiver

 


Broadband Transmitter

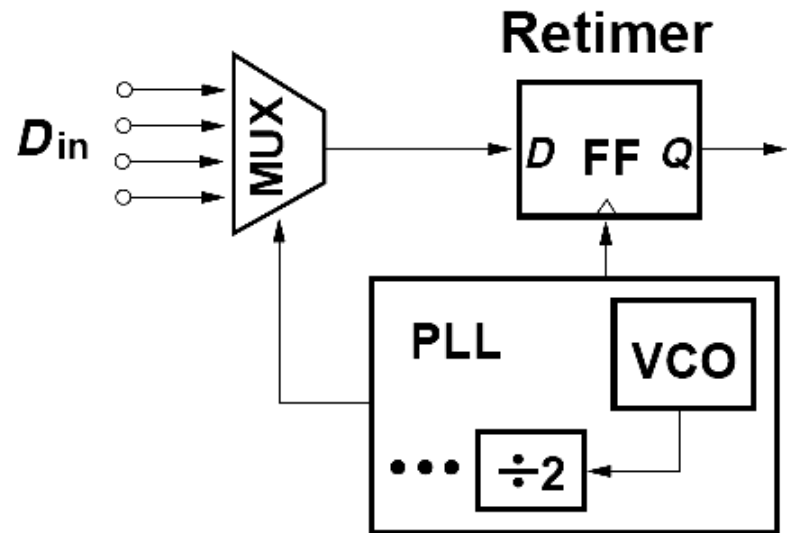

- Half-rate retimer in transmitter would be prone to clock and device asymmetries
 - => Must use a full-rate retimer.
 - => Need a 40-GHz divider.


Full-Rate Divider Applications

Wireless Frontend

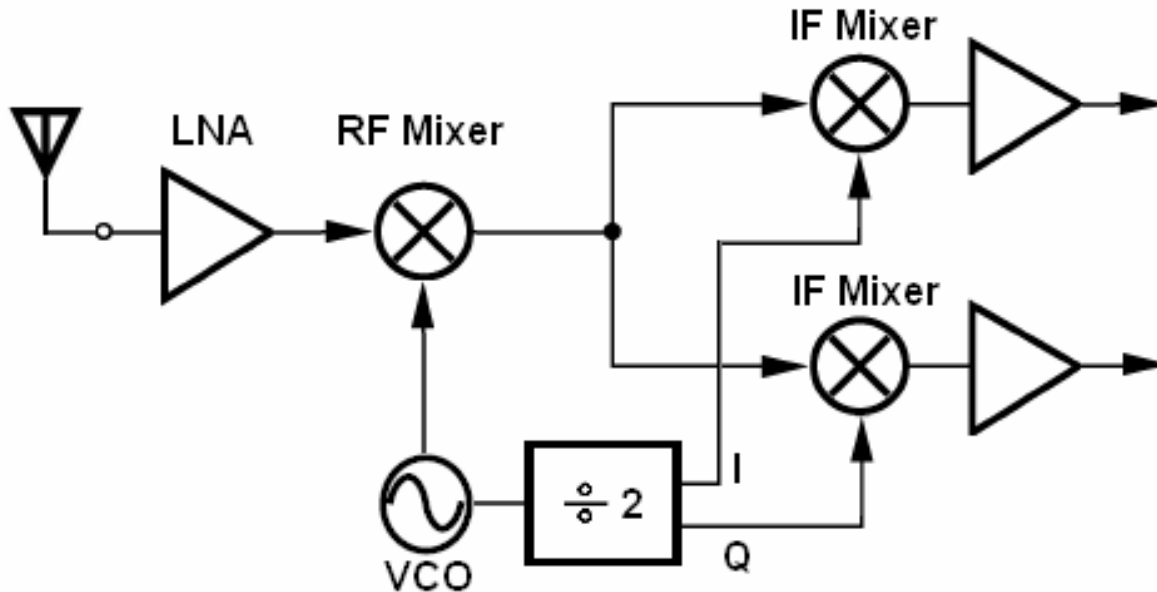

- ❑ **I/Q mismatch of great importance.**
- ❑ **Very high speed.**

Static Dividers


 


- ❑ Edge-triggered flipflop toggle between the two states by “negative feedback”.
- ❑ Wide range of operation (almost from DC to the circuit’s bandwidth).
- ❑ Overlapped clock may cause racing.
⇒ Rising/falling time of CK_{in} matters.



Implementation of Flipflops

□ Almost any type (digital or analog) can serve:

  - Multiplexer-Based
- Pseudostatic
- C²MOS
- TSPC
- CML (Current-Steering)




CML Latch

 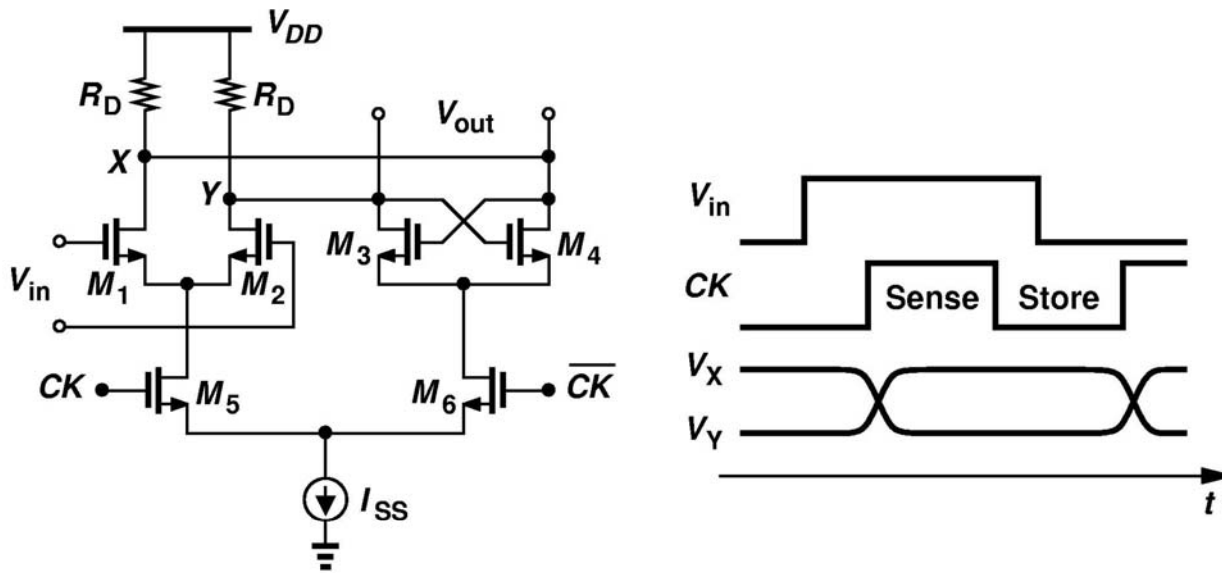


- Speed limited by RC time constant.

Meta-Stability

 


- ❑ Metastable sampling may cause incomplete regeneration, leading to a finite slope at small $\Delta\phi$.
- ❑ Depends on linear gain A_{lin} , regeneration gain A_{reg} , and time constant τ .

Regeneration of Meta-Stable Points

 



- **FF-based divider fails when it can not flip the state in one (input) clock cycle.**

Superdynamic Flipflop

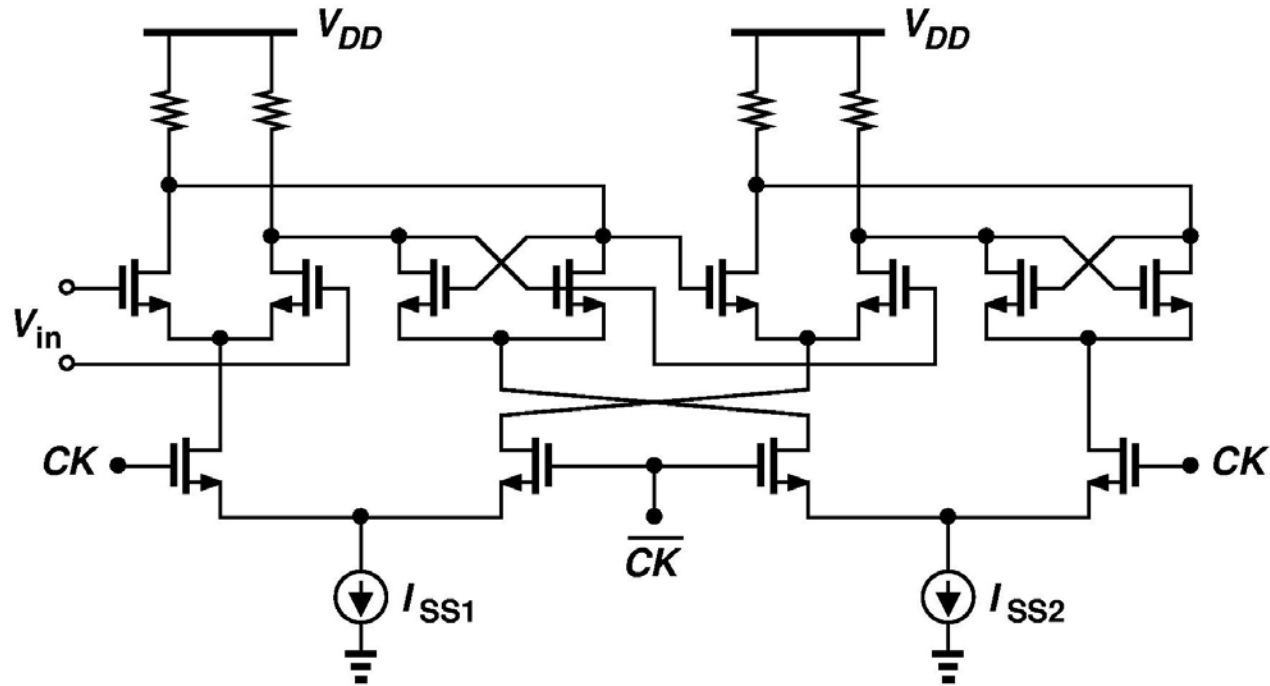

- Allows different current for sampling and regeneration.


Free-Running Frequency

  

- At f_{CK1} the divider behaves as a ring oscillator (with the cross-coupled pair providing sufficient phase shift), and requires little input power.


Static and Dynamic Dividers

Static Divider

 


- ❑ Buffer input capacitance degrades the speed considerably.
- ❑ Speed limited to 18 GHz in 0.18- μm CMOS Technology.

Dynamic (Miller) Divider

 


- ❑ LPF absorbs circuit parasitics \Rightarrow High-speed operation.
- ❑ Circuit must satisfy certain phase shift requirements.

Conventional Dynamic Divider

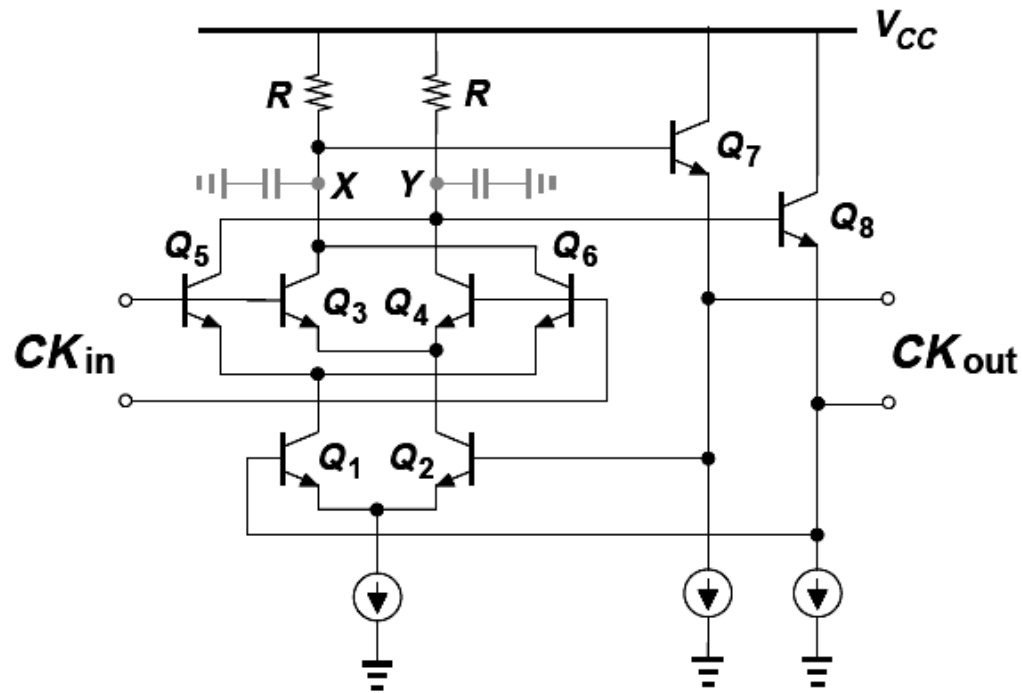

- ❑ Exploits natural low-pass filtering at X and Y .
- ❑ Devices in the loop contribute enough phase shift for startup.
- ❑ But load resistance would consume large voltage headroom in CMOS.

Analysis of Dynamic (Miller) Divider


 


$$R_1 C_1 \frac{dy}{dt} + y = \beta y A \cos \omega_{in} t$$

$$\Rightarrow y(t) = y(0) \exp\left(-\frac{t}{R_1 C_1} + \frac{\beta A}{R_1 C_1 \omega_{in}} \sin \omega_{in} t\right)$$


- ⇒ Decays to zero with a time constant of $R_1 C_1$.
- ⇒ Divider doesn't work without proper delay along the loop.

Analysis of Dynamic Divider

  

- **90° phase shift satisfies the division requirement.**
- **Usually an emitter follower is needed to provide the required phase shift.**

Rough Estimation of Operation Range

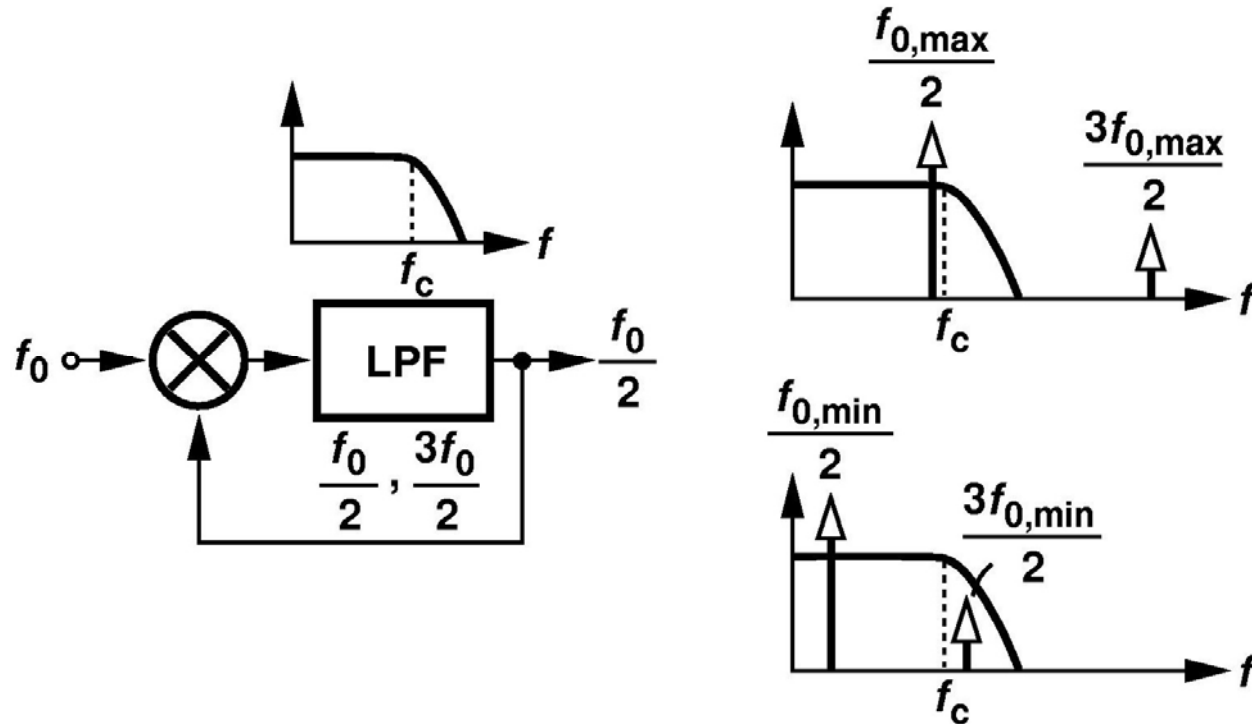


□ The LPF must (1) filter out $\frac{3f_0}{2}$, (2) preserve $\frac{f_0}{2}$.

⇒ $\frac{f_{0,max}}{2} \cong f_c$ and $\frac{3f_{0,min}}{2} \cong f_c$

⇒ $\frac{2f_c}{3} < f_0 < 2f_c$

Dynamic Divider with Bandpass Load

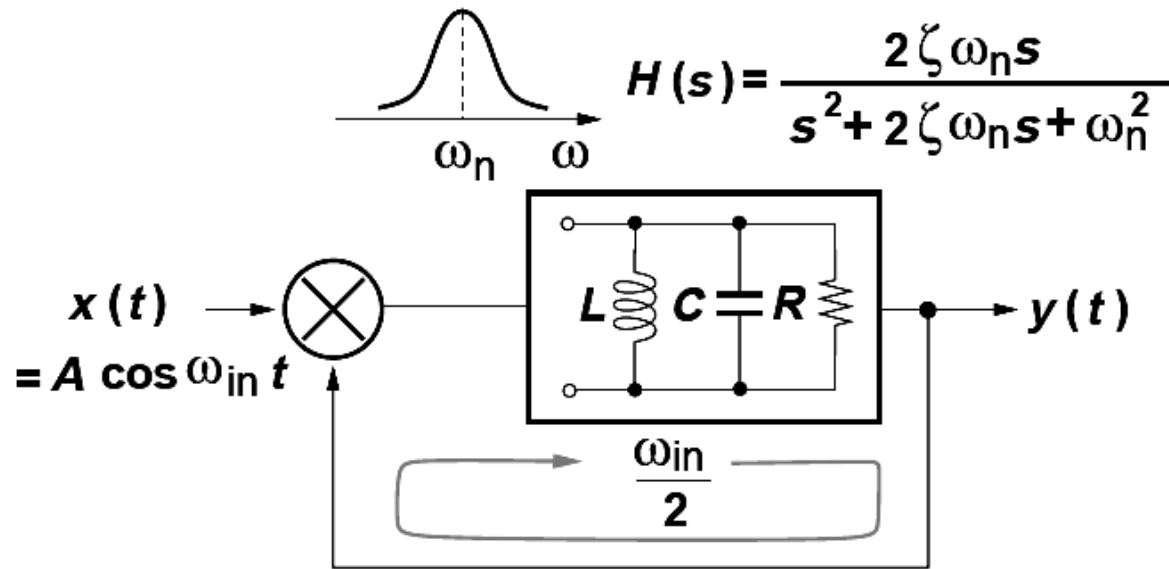

Loop gain requirement:

$$\frac{\beta A}{2} \left| H(j \frac{\omega_{in}}{2}) \right| \geq 1$$

Thus,


$$A \geq \frac{2}{\beta} \sqrt{1 + \frac{(1 - \frac{\omega_{in}^2}{4\omega_n^2})^2}{\zeta^2 \frac{\omega_{in}^2}{\omega_n^2}}}$$

Frequency Range for Correct Division

$$A \geq \frac{2}{\beta} \sqrt{1 + \frac{\left(1 - \frac{\omega_{in}^2}{4\omega_n^2}\right)^2}{\zeta^2 \frac{\omega_{in}^2}{\omega_n^2}}}$$


for $\Delta\omega = |\omega_{in} - 2\omega_n| \ll 2\omega_n$:
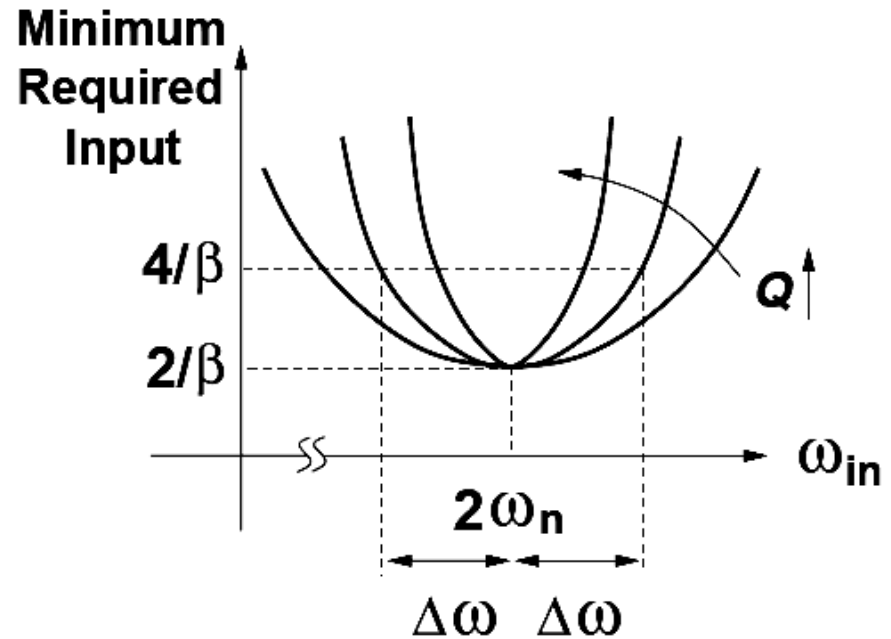
$$A \geq \frac{2}{\beta} \sqrt{1 + \left(\frac{Q\Delta\omega}{\omega_n}\right)^2}$$



For Example, if $A_{\max} = \frac{4}{\beta}$, $\Delta\omega = \frac{\sqrt{3}}{Q} \omega_n$

 Intuitive Understanding of Bandpass Division





$$y \propto \cos \frac{\omega_{in} t}{2} + \alpha \cos \frac{3\omega_{in} t}{2} \quad \Rightarrow \quad 0 < \alpha < 1/3.$$


$$\text{Actually, } \Rightarrow \quad 0 < \alpha < 1/(2\sqrt{3}).$$

Reference: “A 40-GHz Frequency Divider in 0.18-um CMOS Technology”, JSSC, April 2004.

RF-Port and LO-Port Feedback

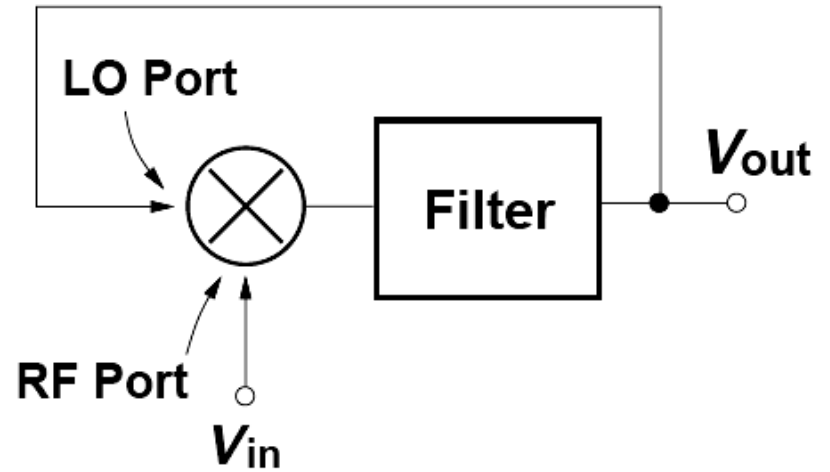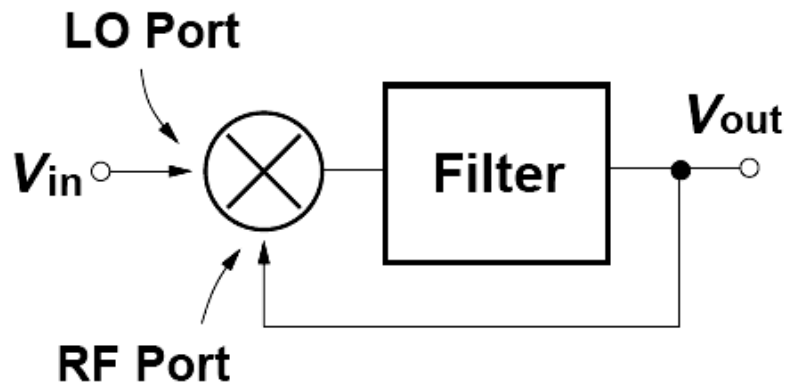

RF-Port Feedback

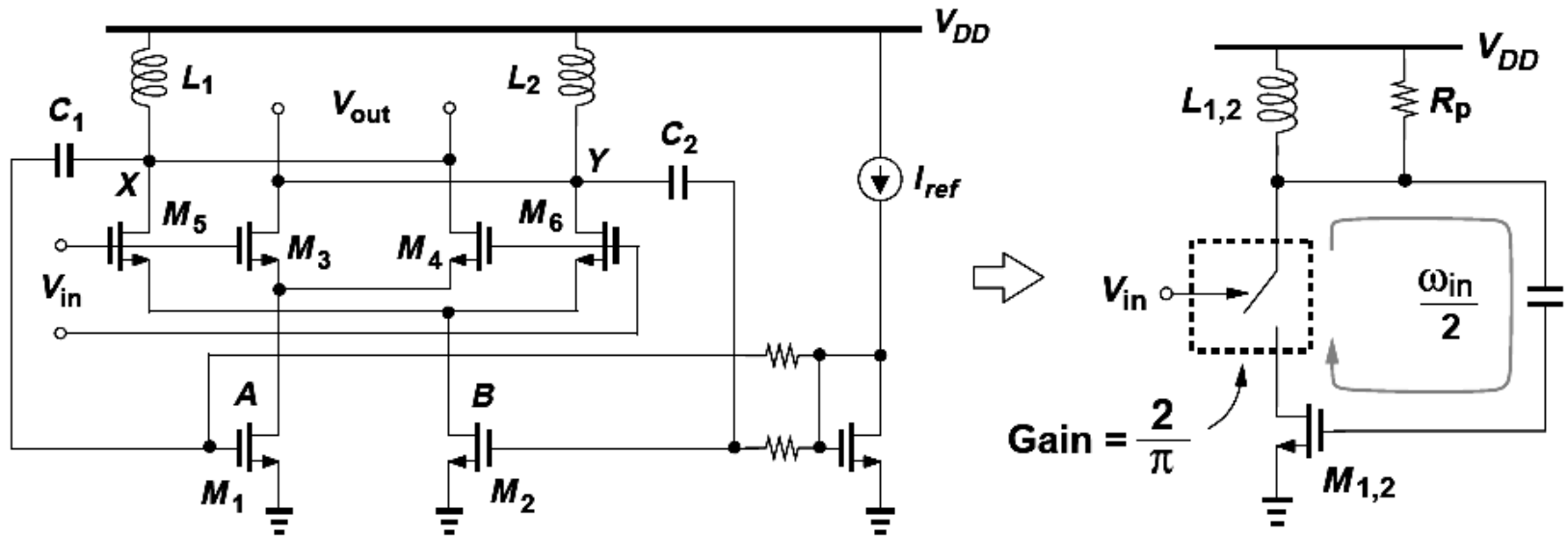


Nonidealities:

- Current Loss at A and B
- Gradual Switching of M_3 - M_6
- Parasitics at X and Y

$$\text{Loop gain} = \frac{2}{\pi} g_{m1,2} R_p$$


$$\begin{cases} R_p = Q L_{1,2} \frac{\omega_{in}}{2} \\ g_m = 2\pi f_T C_{GS} \\ \frac{\omega_{in}}{2} = \frac{3}{\sqrt{C_{GS} L_{1,2}}} \end{cases} \Rightarrow Q = \frac{\pi}{2} \cdot \frac{f_{in}/2}{f_T}$$

LO-Port Feedback

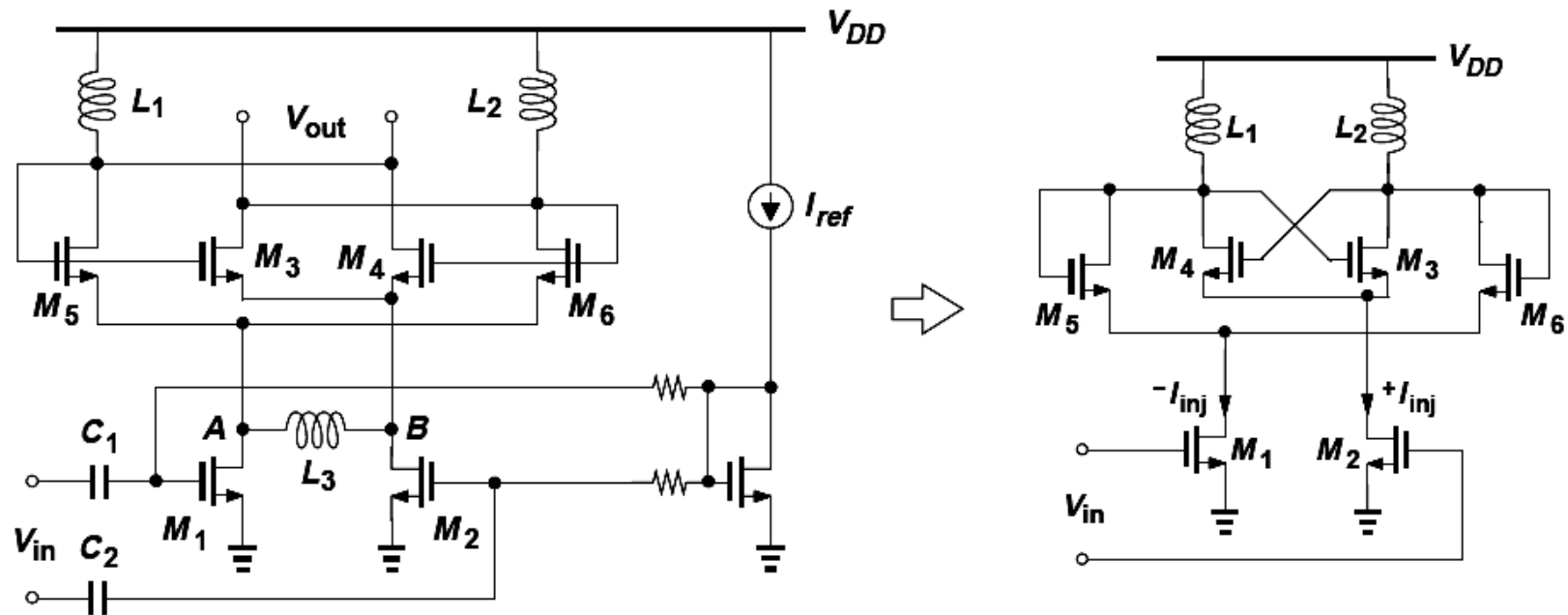

- With feedback applied to LO port, the circuit resembles an injection-locked divider.


Injection-Locked Divider

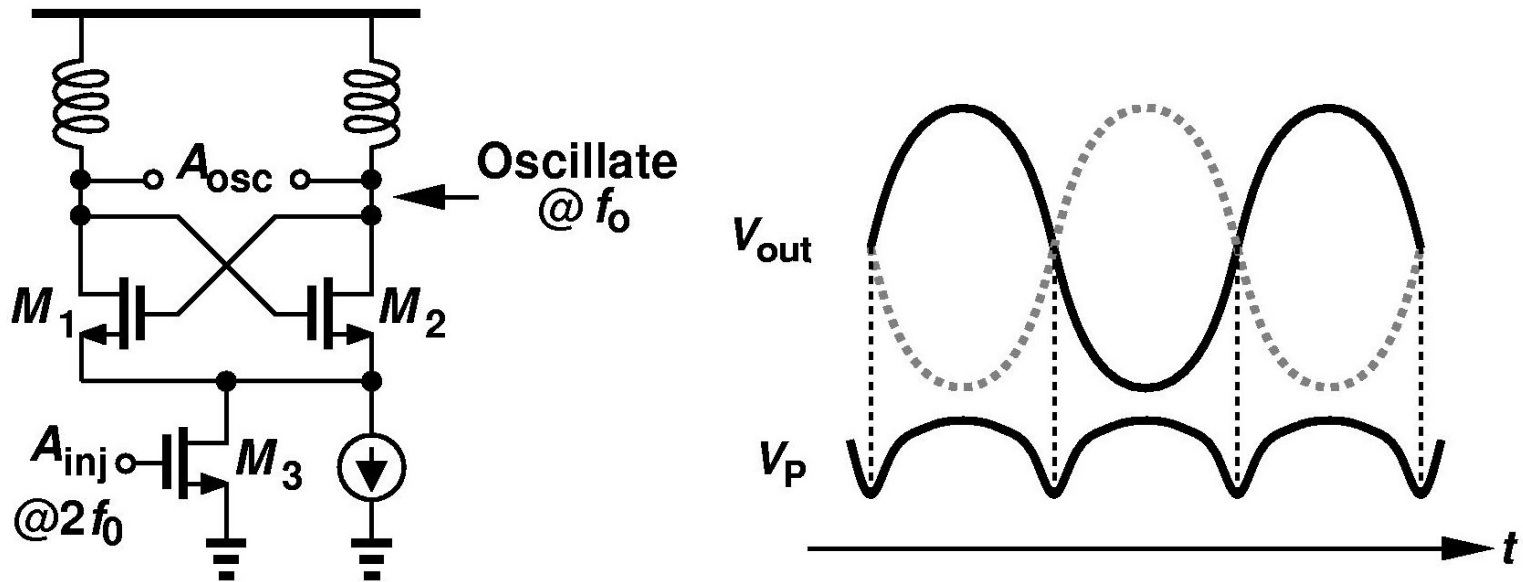

□ Injecting signal at twice the oscillation frequency.

□ Locking range $\cong \frac{f_0}{2Q} \cdot \frac{A_{inj}}{A_{osc}} \cdot \frac{4}{3\pi}$


Modified Injection-Locked Divider

 

- Resonate out parasitic capacitance at node P to allow stronger signal injection to the divider.


Multi-Modulus Divider

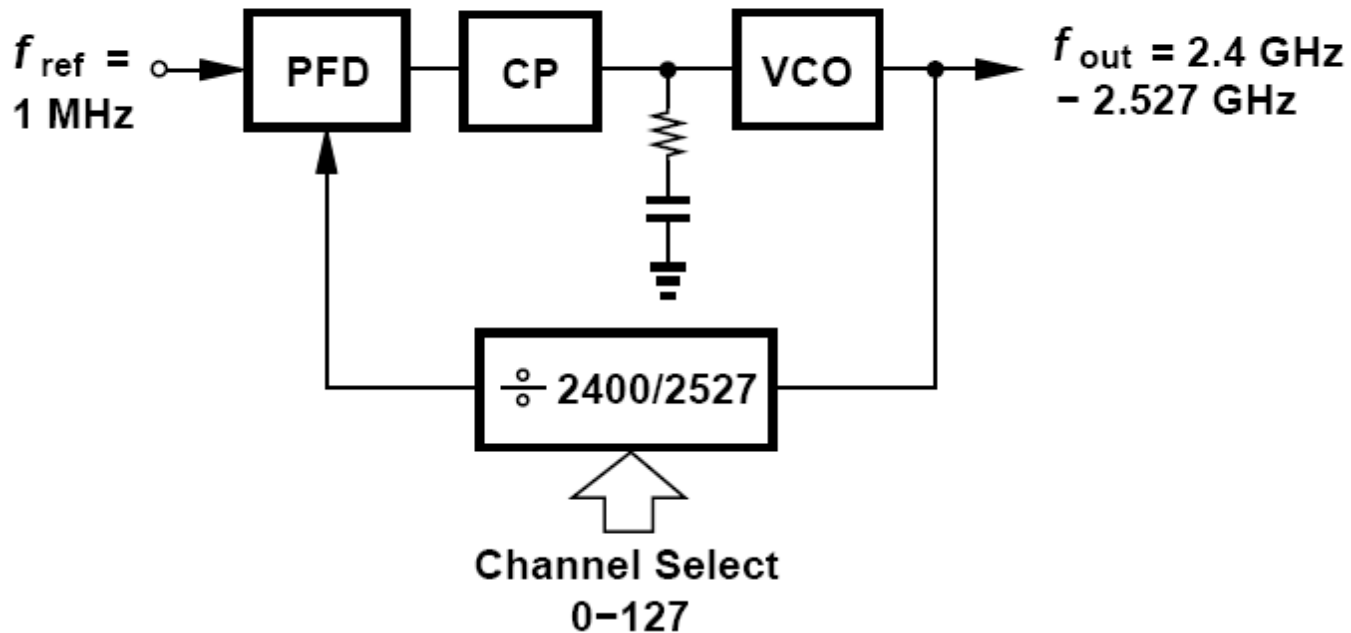- Some applications require programmable division.
- Example: Integer-N Frequency Synthesizer.




Channel Spacing = 1 MHz, Channel Number = 128

Pulse-Swallow Divider

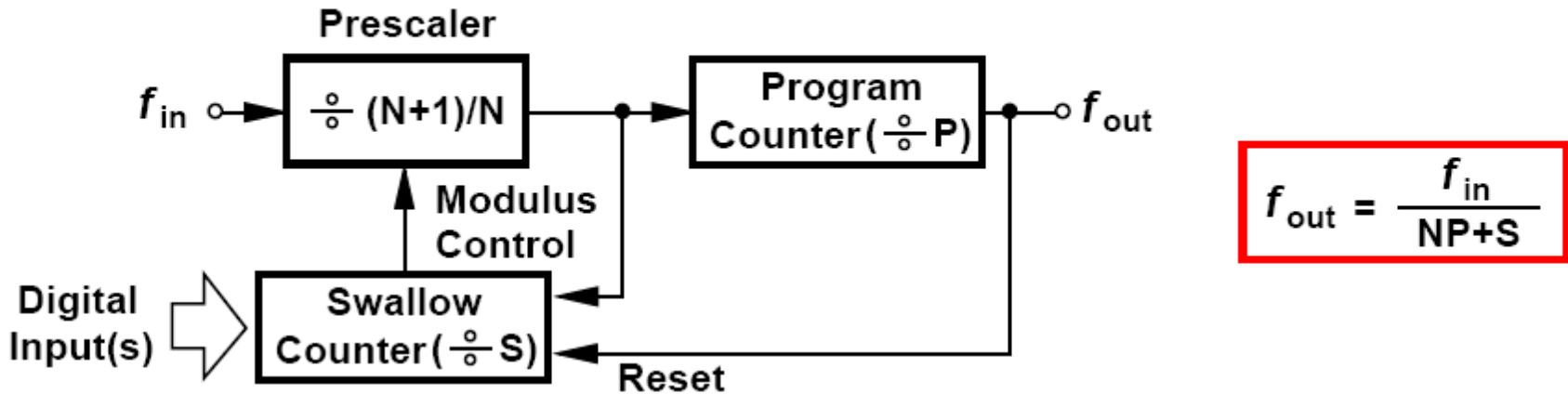

- ❑ Prescaler divides the input frequency by $N+1$ or N based on the modulus control.
- ❑ Program counter divides the prescaler output by P (fixed).
- ❑ Swallow counter divides the prescaler output by S (programmable).



Pulse-Swallow Divider

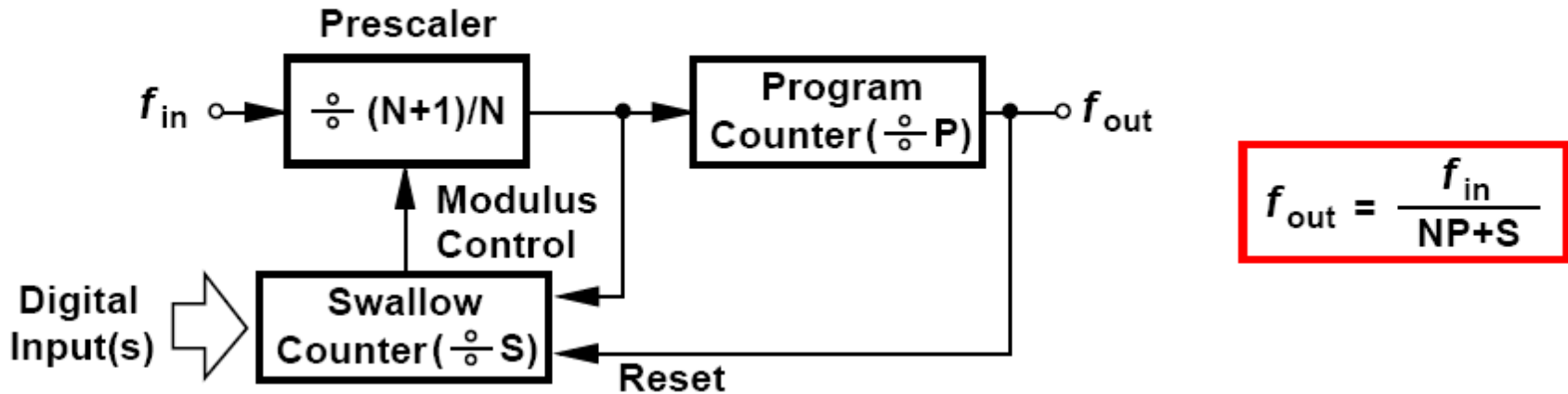

- Start from reset, prescaler divides by $N+1$ until swallow counter is full.
 - After $(N+1)S$ pulses at the input, the modulus control changes to N .
 - Continues to count until program counter is full.
- ⇒ Total pulses at the input = $(N+1)S + N(P-S) = NP + S$.

Prescaler (Dual-Modulus Dividers)


□ $\div 3/2$ Divider

  


□ When $MC=0 \Rightarrow$ OR Gate transparent $\Rightarrow \div 3$

Higher Modulus Prescaler


□ $\div 8/9$ Divider

 

□ $\div 15/16$ Divider

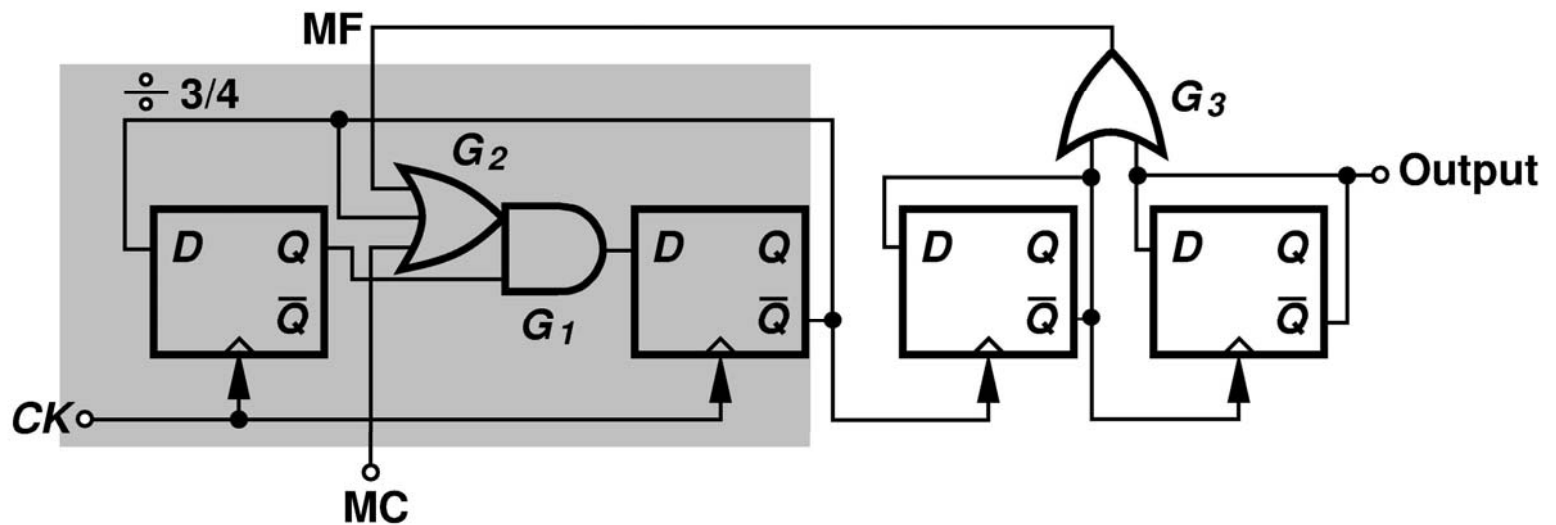

Case Study

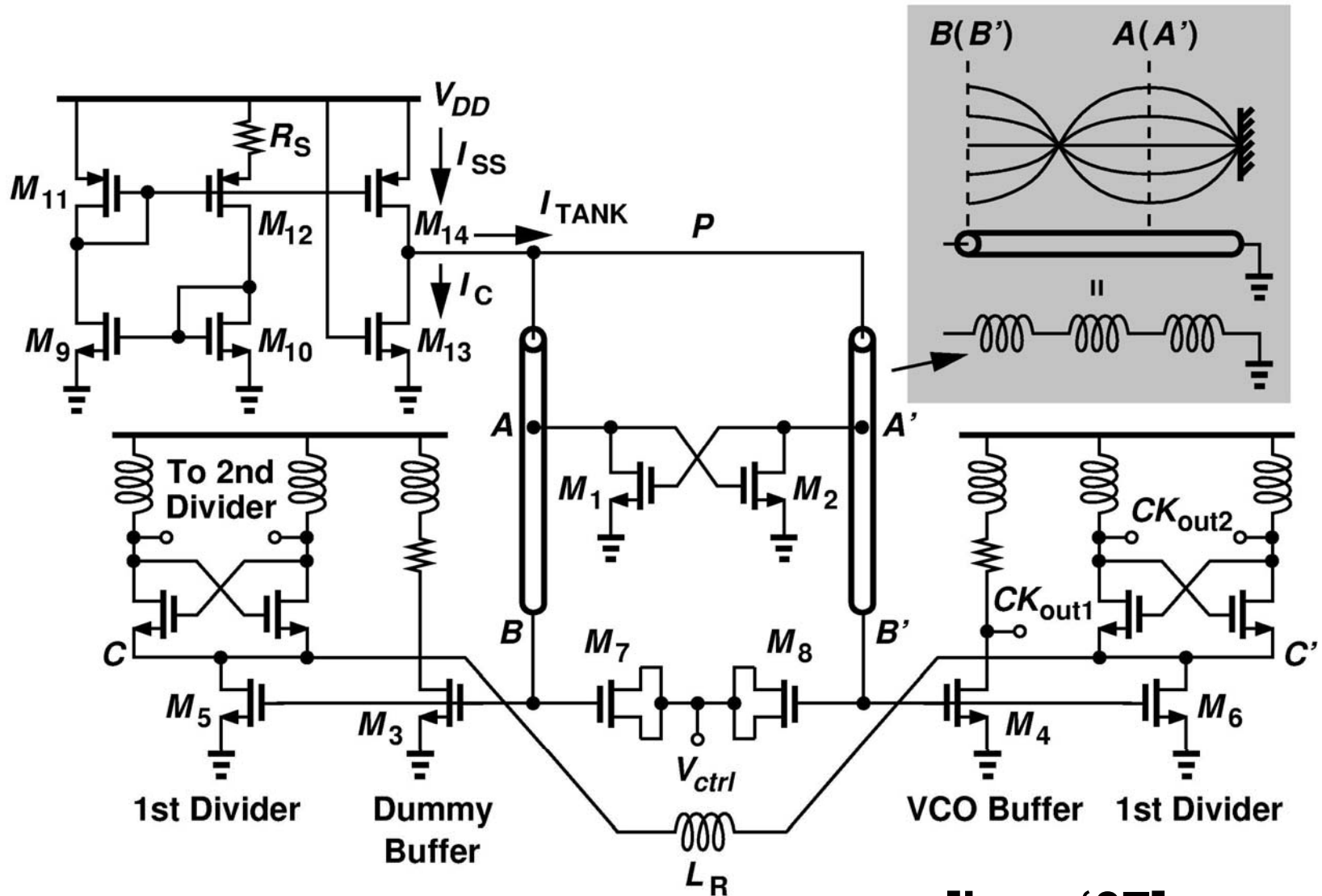

[Lee, '07]